
SPDT 12volt Relay
NAPA AR272

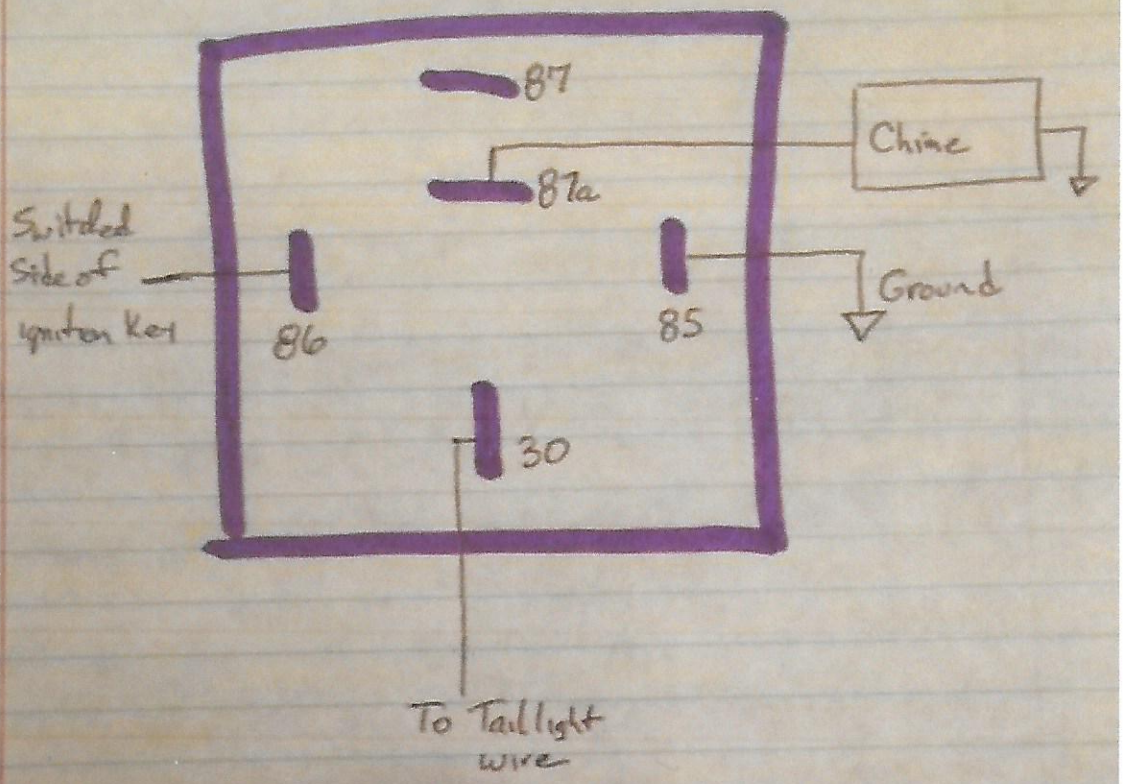

When Power is off at Terminal 86, Terminal 30/87a is close
allowing tail light to power chime

When Power is on at Terminal 86, Terminal 30/87a is ope
no power to chime

Terminal 87 is capped/not used